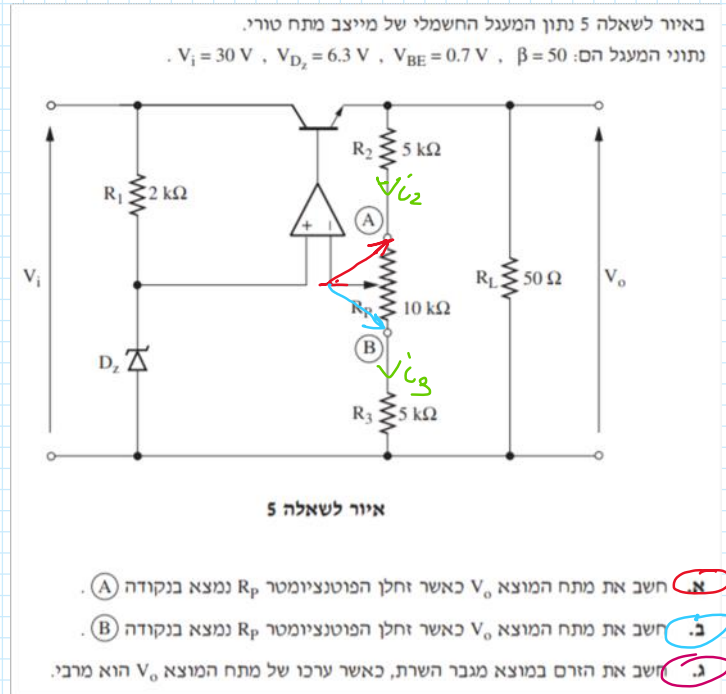




0.7C

$$i_2 = i_3$$

$$\frac{V_o - V_z}{R_2} = \frac{V_z - 0}{R_p + R_3}$$

$$\frac{V_o - 6.3}{5} = \frac{6.3}{10 + 5}$$

$$V_o - 6.3 = \frac{6.3 \cdot 5}{15}$$

$$V_o - 6.3 = \frac{6.3}{3}$$

$$V_o = \frac{6.3}{3} + 6.3$$

$$V_o = 8.4\text{ V}$$

$$I_L = \frac{V_o}{R_L} = \frac{25.2}{50}$$

$$I_L = 0.504\text{ A}$$

$$i_2 = i_3$$

$$\frac{V_o - V_z}{R_2 + R_p} = \frac{V_z - 0}{R_3}$$

$$\frac{V_o - 6.3}{5 + 10} = \frac{6.3}{5}$$

$$V_o - 6.3 = \frac{6.3}{5} \cdot 15$$

$$V_o = (6.3 \cdot 3) + 6.3$$

$$V_o = 25.2\text{ V}$$

0.7C